

Constructing The Double-Quadrature (DQ) Receiver


I now (July 2020) recommend constructing the “Antarctic” version of the receiver, which has proven to be reliable in harsh field conditions on the sea ice of McMurdo Sound and the Ross Ice Shelf.

Those who don't need to measure depth (cave divers) can construct the simplified version of this receiver without the digital readout and the parts needed to make it work, and run it on a single 9V battery or external 12VDC. See the separate page for the Simplified DQ Receiver.




The Antarctic Receiver

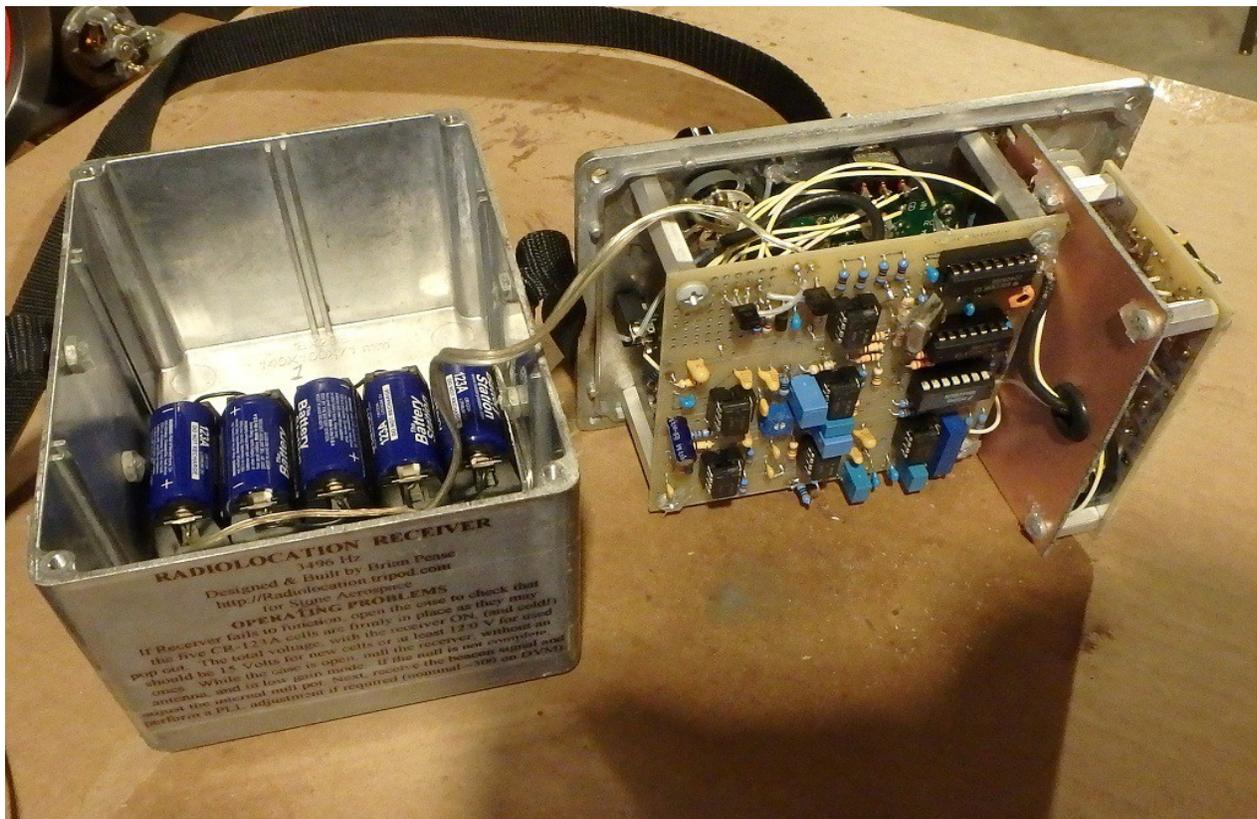This receiver has a gasket on the case and o-rings under the knobs primarily to make the controls “stiff” to prevent movement while walking. Liquid water ingress was not an issue in Antarctica! If common stereo headphones will be used, a stereo jack must be used. It may be wise to install both 1/8” and 1/4” jacks in case of headphone failure.



Interior view of the Antarctic Receiver


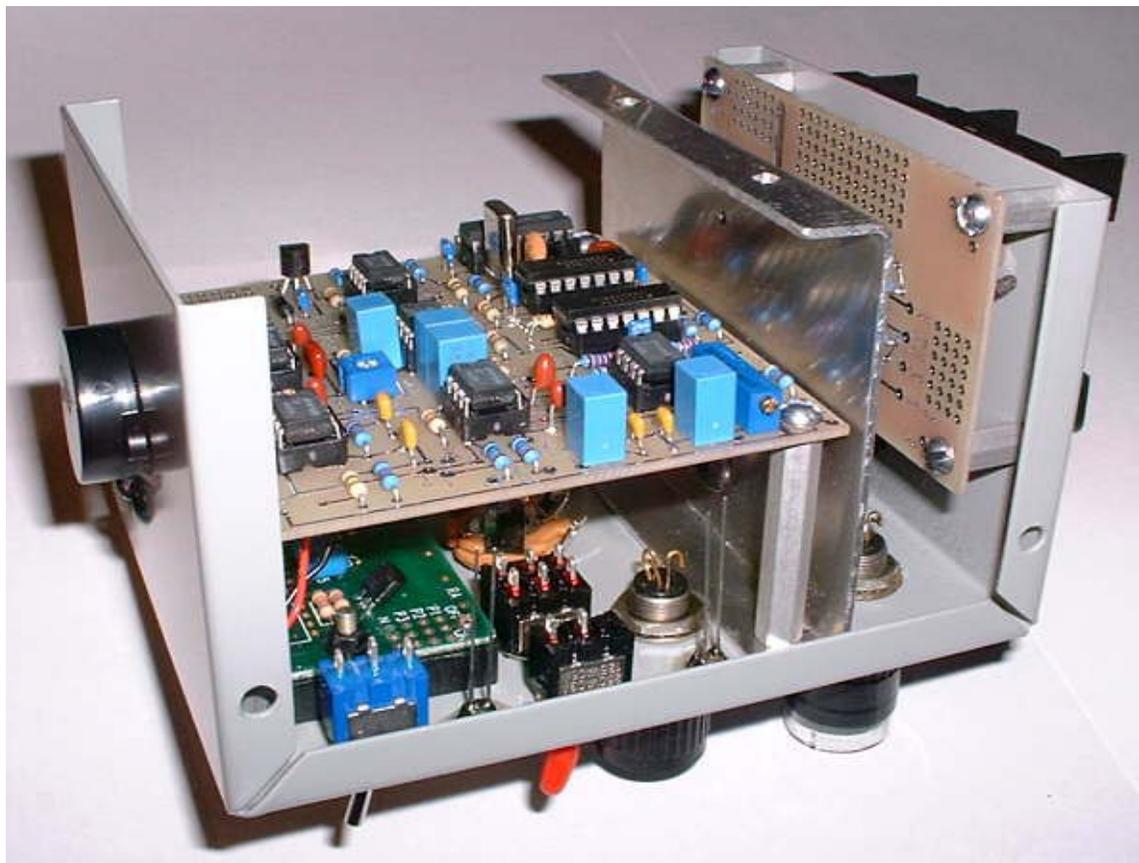


Interior view of DQ receiver in sheet metal box with external batteries


The CR123 cells seem to last forever. The copper clad PC board used as a shield and mount for the RF amp is aligned to fit into the slots in the case. The board is mounted with thin tin-plated steel, which is soldered to the copper and slipped under the mounting spacers for the Main Board. The battery holders are a bit tricky to install. The less common type with wire leads must be used. A layer of duct tape insulates them from the case. The screws must be small 4-40 with “pan” heads that don't stick up much. There must be a closed-cell packing foam spacer over the cells to help hold them in place. It might be better to use a generous amount of top quality double-sided foam tape to hold the holders in place.

See the *DQ Receiver-BeaconPartsLists* for parts advice and ordering, and *Notes on construction and use of the DQ Receiver and Beacon* on the DQ Receiver page of <https://radiolocation.weebly.com> . The latter document includes notes on initial receiver testing and alignment.


A B&W image of the 3 PC boards showing the parts placement is shown below. This includes parts on the detector board that likely will not be installed such as parts for the alarm and the regulator for certain DVM models, U12. Use this guide when mounting parts as there is no silkscreen printing on the board, just some part numbers in copper. Be very careful to place the parts in the correct holes as there are many “vias” (holes) that connect traces from top to bottom that are large enough for component wires! Color images showing both top and bottom traces are included for reference. Here you will just be working with the detector and RF amp boards. There is extra “prototype” space on both boards to add extra features.

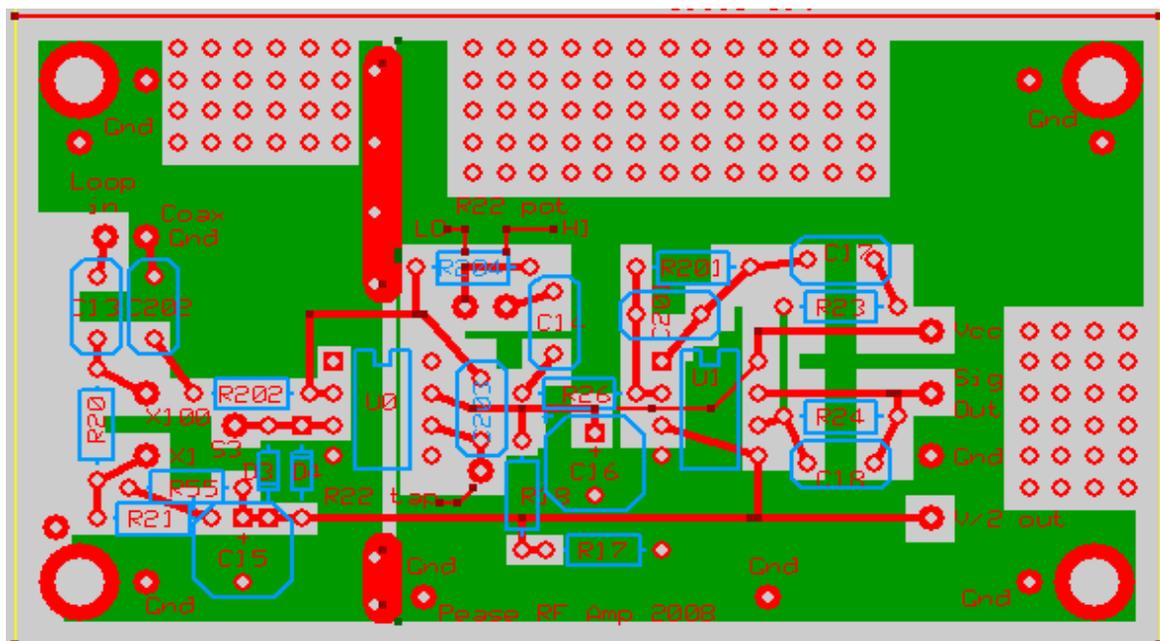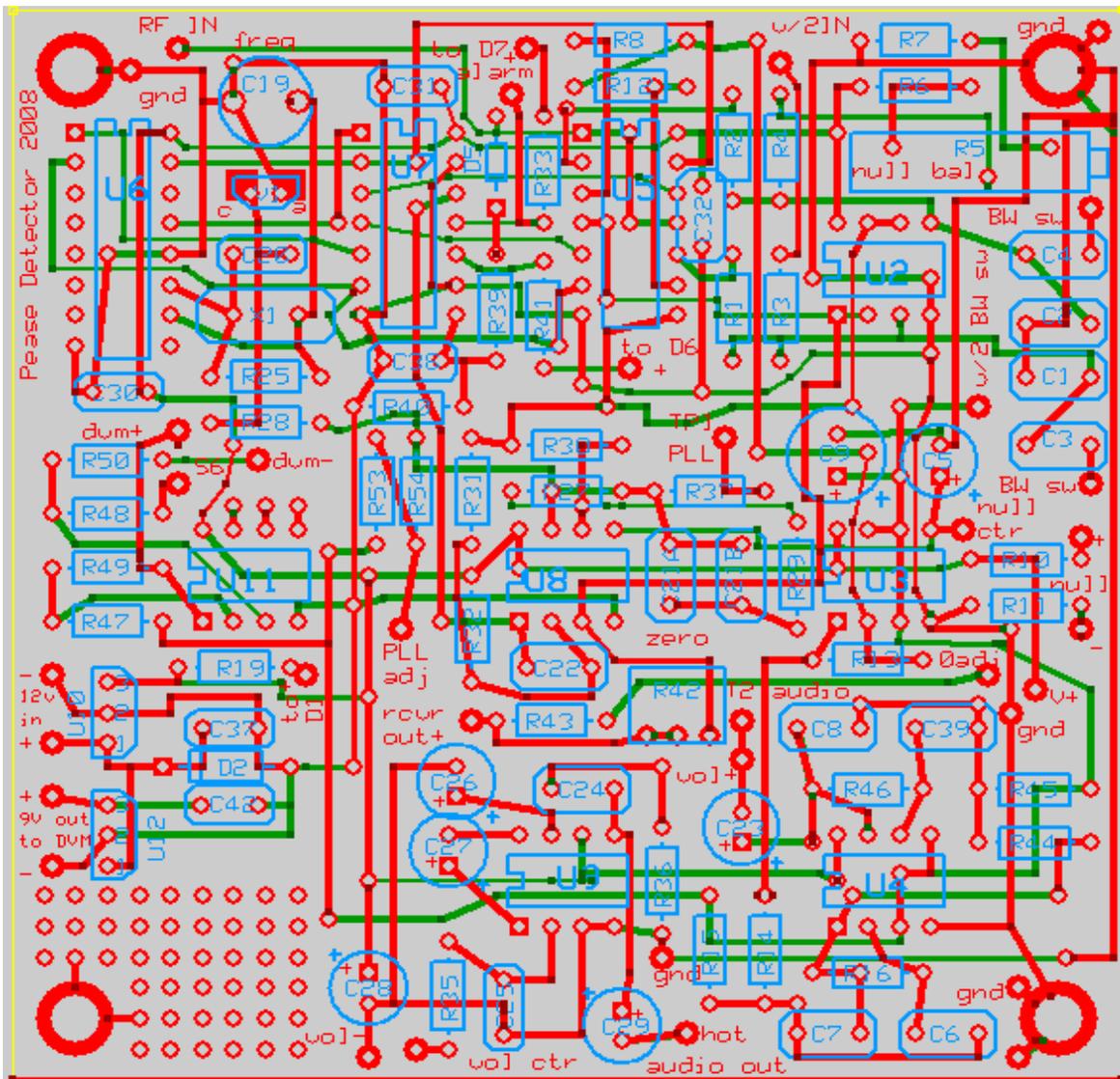


The front panel wiring diagrams are shown below. Small coax cable is used to route the RF signal from the RF Amp board. S4, and the piezo buzzer form the alarm, but are optional. The DVM shown is the general purpose PM-128E that I can supply. I will configure it and test it. It will just need the addition of C40, R51A, and R51B. Any headphones can be used, but I recommend the kind that block outside sound. Higher impedance phones like the mono Telex 600 "language lab) phones I can supply have less feedback to the loop antenna than common 32 Ohm stereo phones. The stereo phones are more comfortable and block more outside noise. Note that the Telex phones will not function in a stereo 1/4" jack unless just the tip contact is wired, otherwise the audio amp will be shorted out. Once the receiver is complete, and you have a working beacon as a signal source, consult the *Notes on Construction and use of the DQ Receiver and Beacon* for initial receiver tests and adjustments.

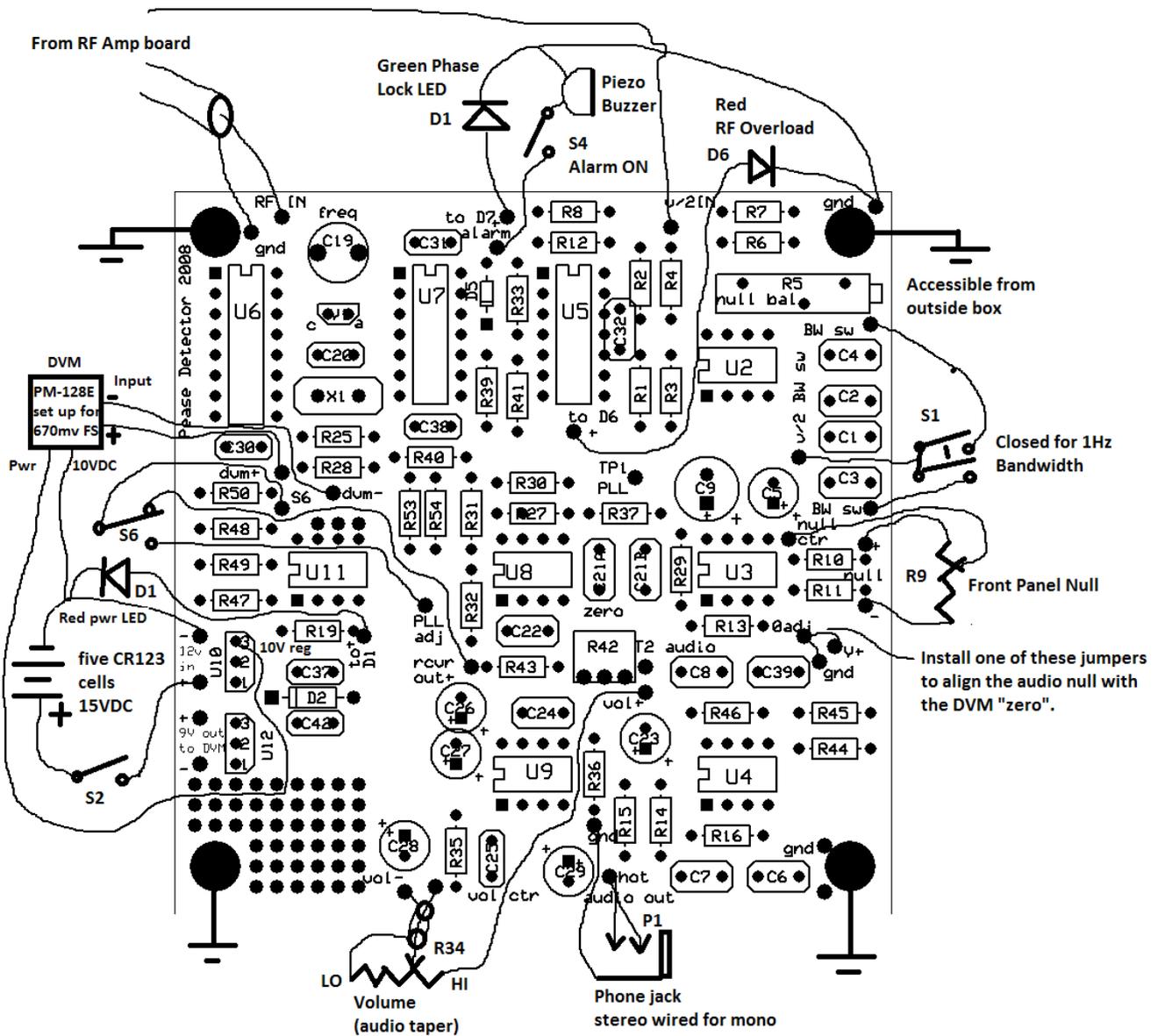

Detector Board Front Panel Wiring

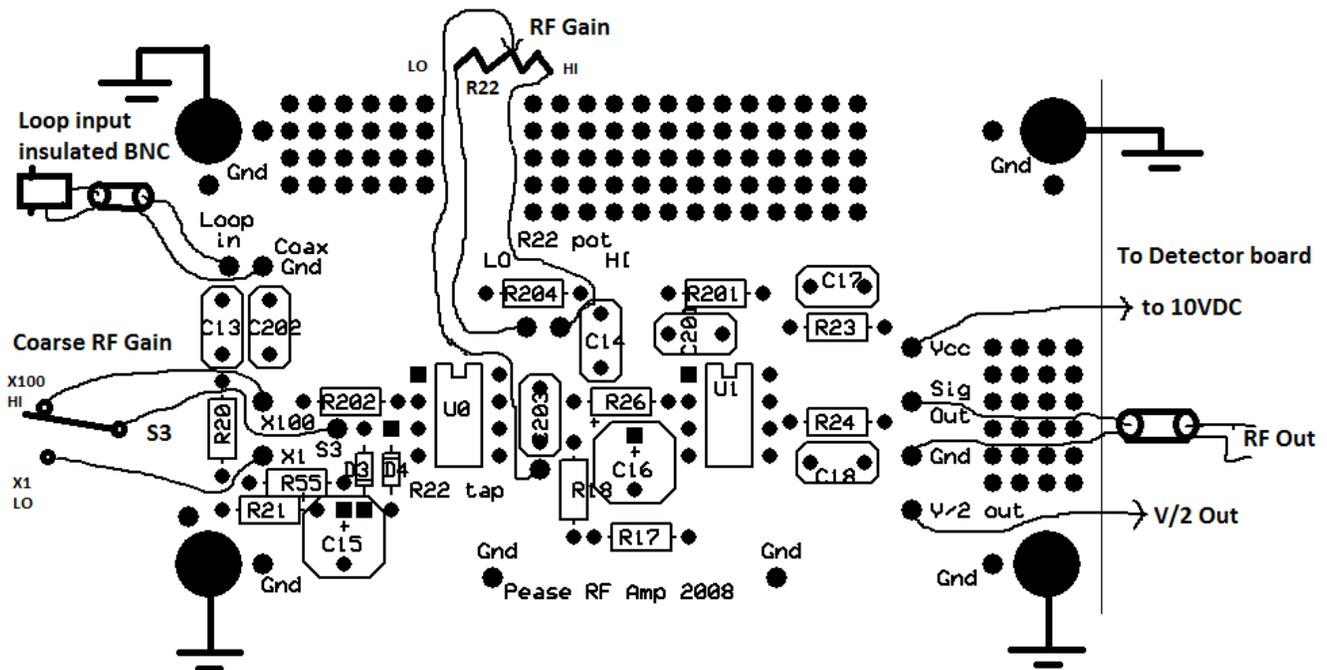


RF Amp Front Panel Wiring

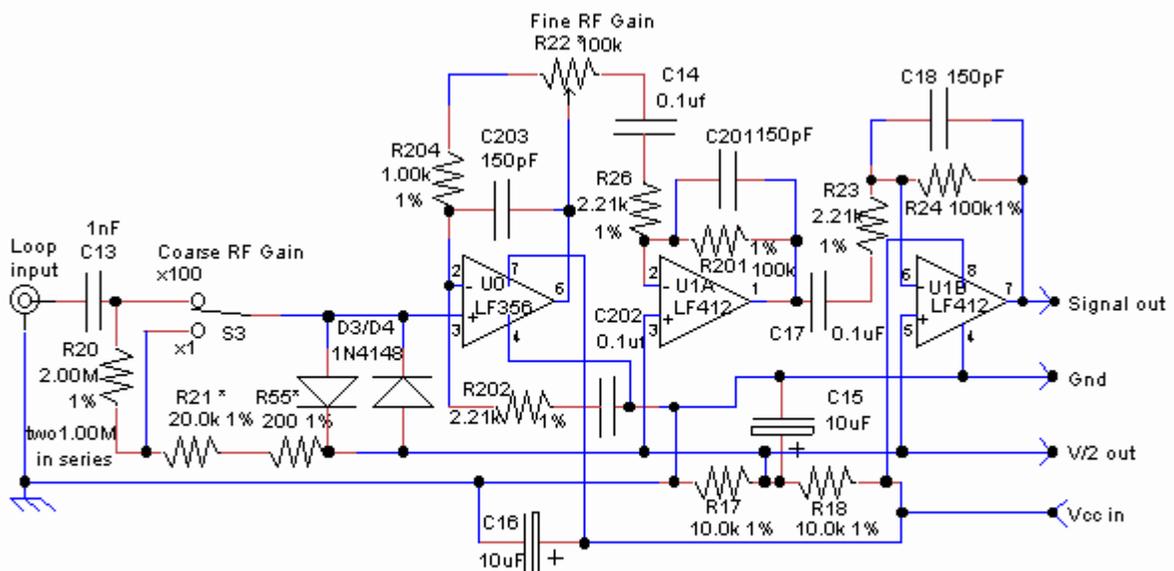

* If "absolute" calibration is desired, R21/R55 should be trimmed to make the attenuation precisely 100:1 and R22 must be a precision 10-turn linear pot with calibrated dial.

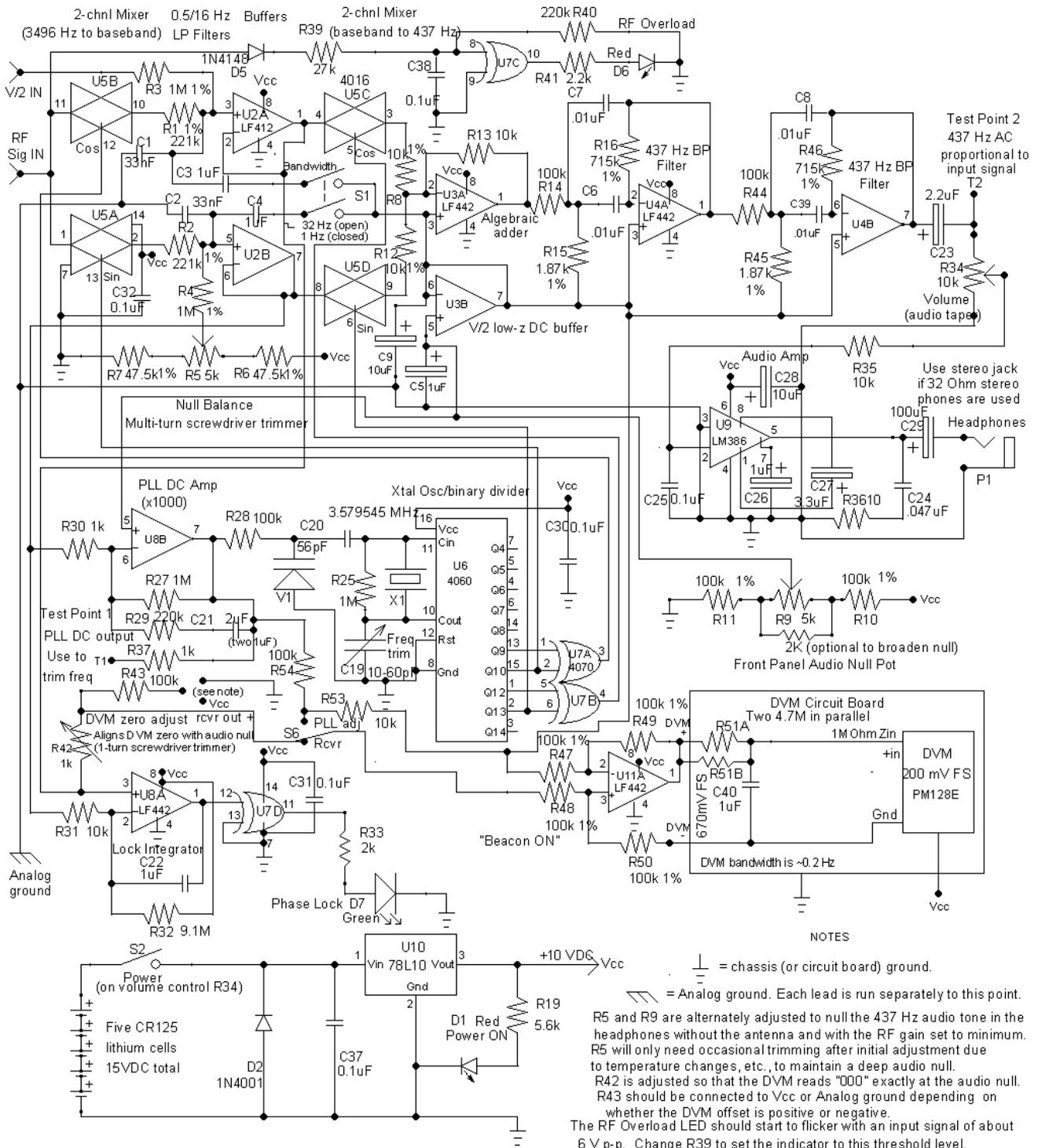RF Amplifier for 3496 Hz DQ Beacon Receiver



Adjust C19 (slowly) until the receiver phase-locks on a moderately strong beacon signal. Next, monitor the DC voltage at Test Point T1. Center the PLL by adjusting C19 VERY slowly until T1 is roughly Vcc/2. If the beacon is fixed-tuned (no trimcap), C19 will seldom if ever require readjustment. Change S6 to PLL adjust and note the value (including polarity) for use in field adjustment.

DQ Receiver Main Board (Detector)

NOTES

⊥ = chassis (or circuit board) ground.

⏏ = Analog ground. Each lead is run separately to this point.

R5 and R9 are alternately adjusted to null the 437 Hz audio tone in the headphones without the antenna and with the RF gain set to minimum. R5 will only need occasional trimming after initial adjustment due to temperature changes, etc., to maintain a deep audio null. R42 is adjusted so that the DVM reads "000" exactly at the audio null. R43 should be connected to Vcc or Analog ground depending on whether the DVM offset is positive or negative.

The RF Overload LED should start to flicker with an input signal of about 6 V p-p. Change R39 to set the indicator to this threshold level. Overload is only a concern when using the DVM for depth measurements.

Title		
DQ Antarctic Receiver Main Ckt Board		
Author		
Brian Pease		
Thru-the-Earth Radiolocation		
File	Document	
\TinyCadDesigns\DQmainboardNewRcvr2020.dsn		
Revision	Date	Sheets
2.0	18 July 2020	1 of 1

Loop Antennas for the DQ Receiver

All DQ receivers can use the same loop antennas for receiving. All are simple parallel tuned L-C circuits fed with RG58 or RG174 (my favorite) coax. Larger loops with more weight of copper wire work best, although small ferrite rod loops are very useful also. Aim for 100k Ohms or greater at resonance so that the thermal noise of the loop overcomes the receiver noise. See the *Receiver Loop Notes* in the *Notes on Construction and use of the DQ Receiver and Beacon* for 3 receive loops I have used. The aluminum bicycle rim loop is shown in the Antarctic photos. My 22 inch loop is shown below. The white cord on the front of the loop is the 6 ft cord (with a bar to step on) used for ratiometric depth measurement.

See *Building the Simplified DQ Receiver* for a very simple loop to build.

